

Custom Computing: Assessed Course Work

Issued date: 8 February 2023

Submission date: 23 February 2023 (submission through CATE)

Include Ruby programs, simulation commands and their results in your written submission for questions 1 and 2, which should also contain appropriate explanations and illustrations. The submission should contain TWO files: (a) one zipfile containing all your Ruby designs and simulation results; (b) one SINGLE PDF file which contains your written submission, including the diagrams and other explanation not in the comments. Both should be submitted via CATE.

1. A design $P1$ can be expressed in the Ruby language as:

$$\begin{aligned} P1 &= Q1^n; fork^{-1} \\ Q1 &= \text{snd.fork}; rsh; [add, D^{-1}] \end{aligned}$$

where $Q1 : \langle in, out \rangle \sim \langle out, in \rangle$.

- (a) Given that add describes a 2-input adder and D^{-1} describes a D register, define the wiring component rsh , and provide a diagram of $P1$ when $n = 4$. Include symbolic simulation for $P1$ when $n = 4$. (10%)
- (b) Use the transformation (no need to include its proof)

$$(A; B)^n = A^n; B^n \quad \text{provided } A; B = B; A,$$

to derive a design $P2$ by inserting registers between the adders. Express $P2$ in the form $Q2^n; fork^{-1}$ and find a suitable definition for $Q2$. Provide a diagram of $P2$ when $n = 4$. Include symbolic simulation for $P2$ when $n = 4$. (15%)

- (c) Using slowdown and the transformation in Part (b), derive a fully-pipelined design $P3$ based on $P1$. Express $P3$ in the form $Q3^n; fork^{-1}$ and find a suitable definition for $Q3$. Provide a diagram of $P3$ when $n = 4$. Include symbolic simulation for $P3$ when $n = 4$. (15%)

Note: in Parts (b) and (c), you may put balancing antidelays on the range of the $fork^{-1}$.

2. (a) Given that $[P, Q]; R = R; Q$, show by induction that $[P, Q]^n; R = R; Q^n$. (20%)
- (b) For $n > 0$, provide inductive definitions for $\text{rdr}_n R$ and $\Delta_n R$. (2%)
- (c) Horner's Rule is given by:
if $[P, Q]; R = R; Q$ then $[\Delta_n P, Q^n]; \text{rdr}_n R = \text{rdr}_n (\text{snd } Q; R)$.
Provide diagrams for the circuit described on the left-hand side and the circuit described on the right-hand side of this equation when $n=3$. (6%)
- (d) What are P , Q and R when Horner's Rule is applied to optimise polynomial evaluation? Check your answer by symbolic simulation of a polynomial evaluation design with the coefficients $a0, a1, a2, a3$. (12%)
3. Write a Maxeler MaxJ kernel to calculate N -dimensional vector dot product (inner product), given $2N$ inputs $a1, a2, \dots, aN$ and $b1, b2, \dots, bN$. Your design should output one dot product per cycle. Omit the class declaration and import statements. Assume that N is available as a parameter. (20 %)